 


CS2022 Bus-based Transfers

- ▶ Digital systems typically have a considerable number of registers N .
- ▶ Typically $8 \leq N \leq 256$
- ▶ Programmer need to be able to make transfers between any pair of them.
- ▶ Let us consider the $N=3$ and use 2:1 MUXs to interconnect $R0, R1, R2$.
- ▶ The result is on the next slide.

CS2022

Register Transfer via MUX Diagram




CS2022 Register Transfer via MUXs

- ▶ This is a very flexible system for it can make up to three independent transfers in one clock period.

RT	S2 S1 S0	L2 L1 L0	Description
$R2 \leftarrow R1$	1 X X	1 0 0	Point-to-Point
$R2 \leftarrow R1, R1 \leftarrow R2$	1 1 X	1 1 0	Reg. Exchange
$R2 \leftarrow R1, R1 \leftarrow R0$ $R0 \leftarrow R2$	1 0 0	1 1 1	Reg. Rotate
$R2 \leftarrow R0, R1 \leftarrow R0$	0 0 X	1 1 0	Reg. broadcast

- ▶ But this is very costly in terms of interconnect, requiring $6 \cdot n$ MUX input connections.
- ▶ To connect $N \cdot n$ -bit registers will require $(N-1) \cdot N \cdot n$ wires.

CS2022 Register Transfer via MUX & Bus

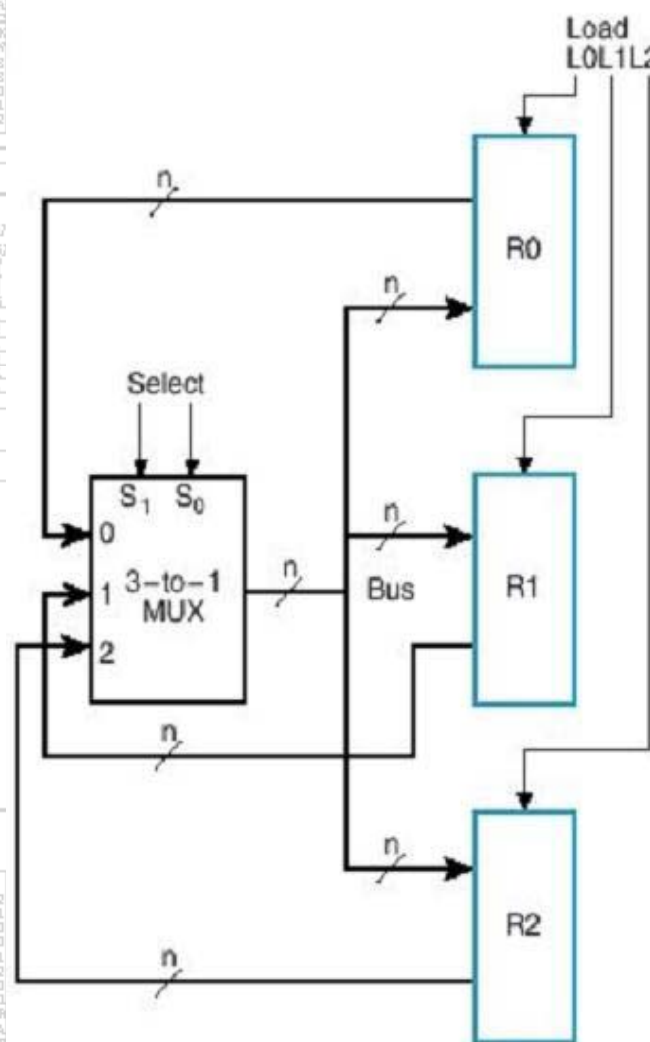

► To reduce the amount of interconnects we can use 3-1 MUXs with a single MUX-to-Register bus connection.

Register Transfer via 3-1 MUXs and MUX-to-Register Bus




- ▶ This results in the loss of some flexibility:

RT	S1 S0	L2 L1 L0	Description
$R0 \leftarrow R2$	1 0	0 0 1	Point-to-Point
$R0 \leftarrow R1, R2 \leftarrow R1$	0 1	1 0 1	Reg. Broadcast
$R0 \leftarrow R1, R1 \leftarrow R0$	IMPOSSIBLE		Single source only


- ▶ But the MUX input connections have reduced from $6*n$ to $3*n$.
- ▶ For N Register we need only $N*n$ wires.

CS2022 Tri-state Bus

   - ▶ Tri-state buffers provide the means to construct a wired-or of arbitrary fan-in, with which we can effectively disperse the MUX on the previous slide right back to the register latches. That is we build our 3:1 MUX as:



CS2022 Tri-state-bus vs. MUX-bus

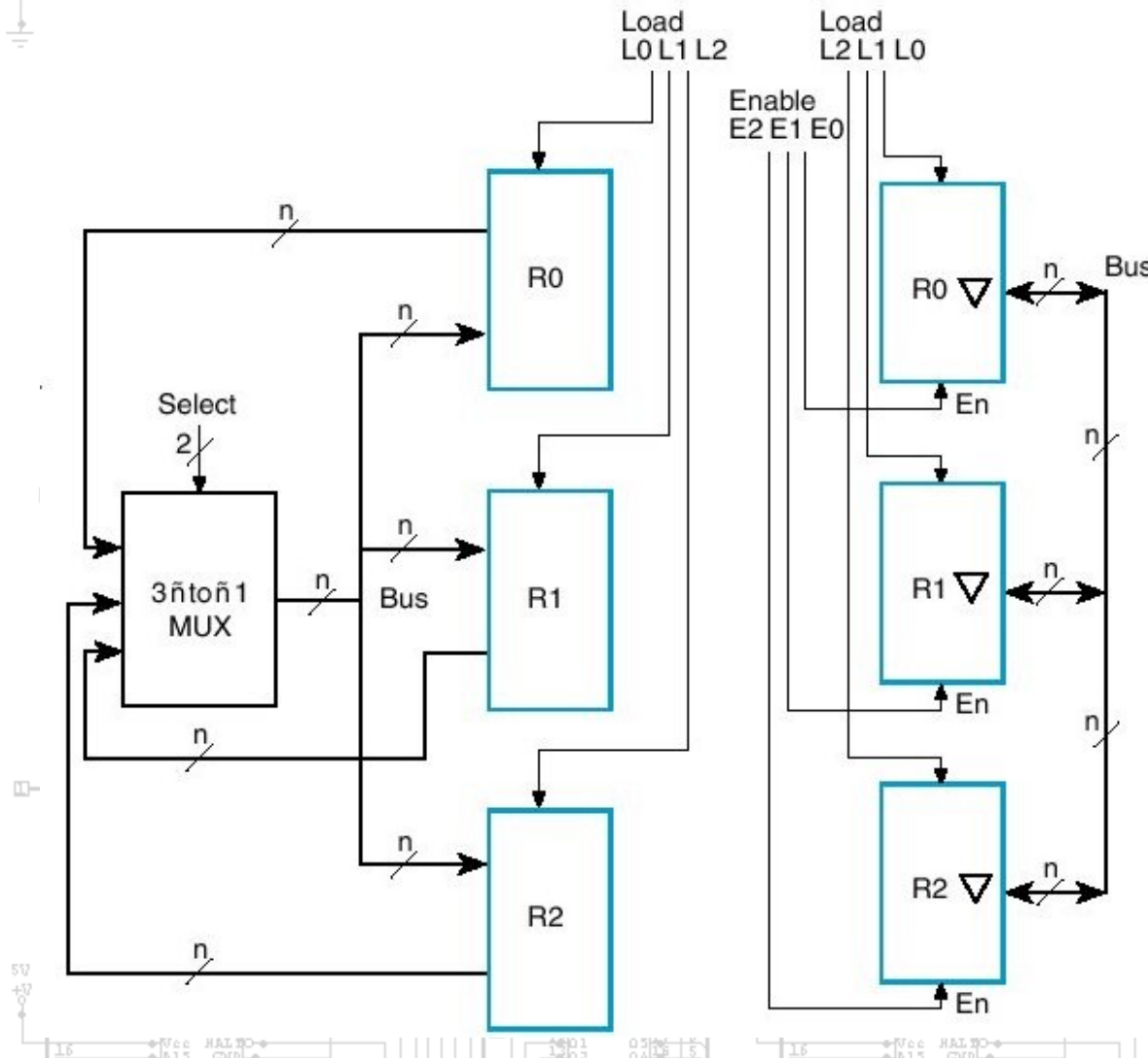


- ▶ This results in a solution seen on the right (tri-state), which has the same functionality as the MUX based solution on the left, using just a single bi-directional bus.

CS2022 Bi-directional Tri-state Bus

<u>RT</u>	<u>E2 E1 E0</u>	<u>L2 L1 L0</u>	<u>Description</u>
$R0 \leftarrow R2$	1 0 0	0 0 1	Point-to-Point
$R0 \leftarrow R1, R2 \leftarrow R1$	0 1 0	1 0 1	Reg. Broadcast
$R0 \leftarrow R1, R1 \leftarrow R0$	IMPOSSIBLE		Single source only

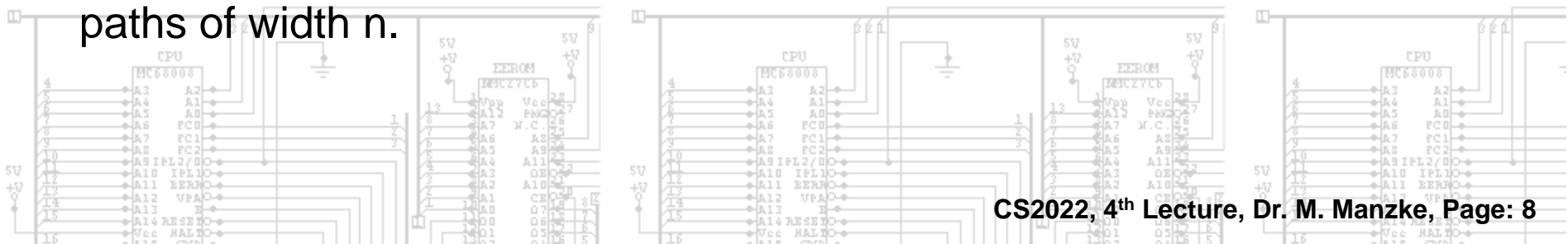- With this arrangement it is possible to connect $N \cdot n$ -bit register with $N-1$ paths of width n .




CS2022 Memory Transfers

- ▶ Typically processor memories are addressed by a number of address registers:
 - ▶ **PC, MAR, IOR**
- ▶ Address register information is transmitted over an address bus to memory **M**.
- ▶ Similarly data is transferred to/from a number of data registers over a data bus.
 - ▶ **Data register: IR, DR, BUF**
- ▶ The schematic on the next slide illustrates how we may organise three address register **A**, selected by **I**, and data register **D**, selected by **J**, to implement read/write on memory **M**.

CS2022

READ:
WRITE:

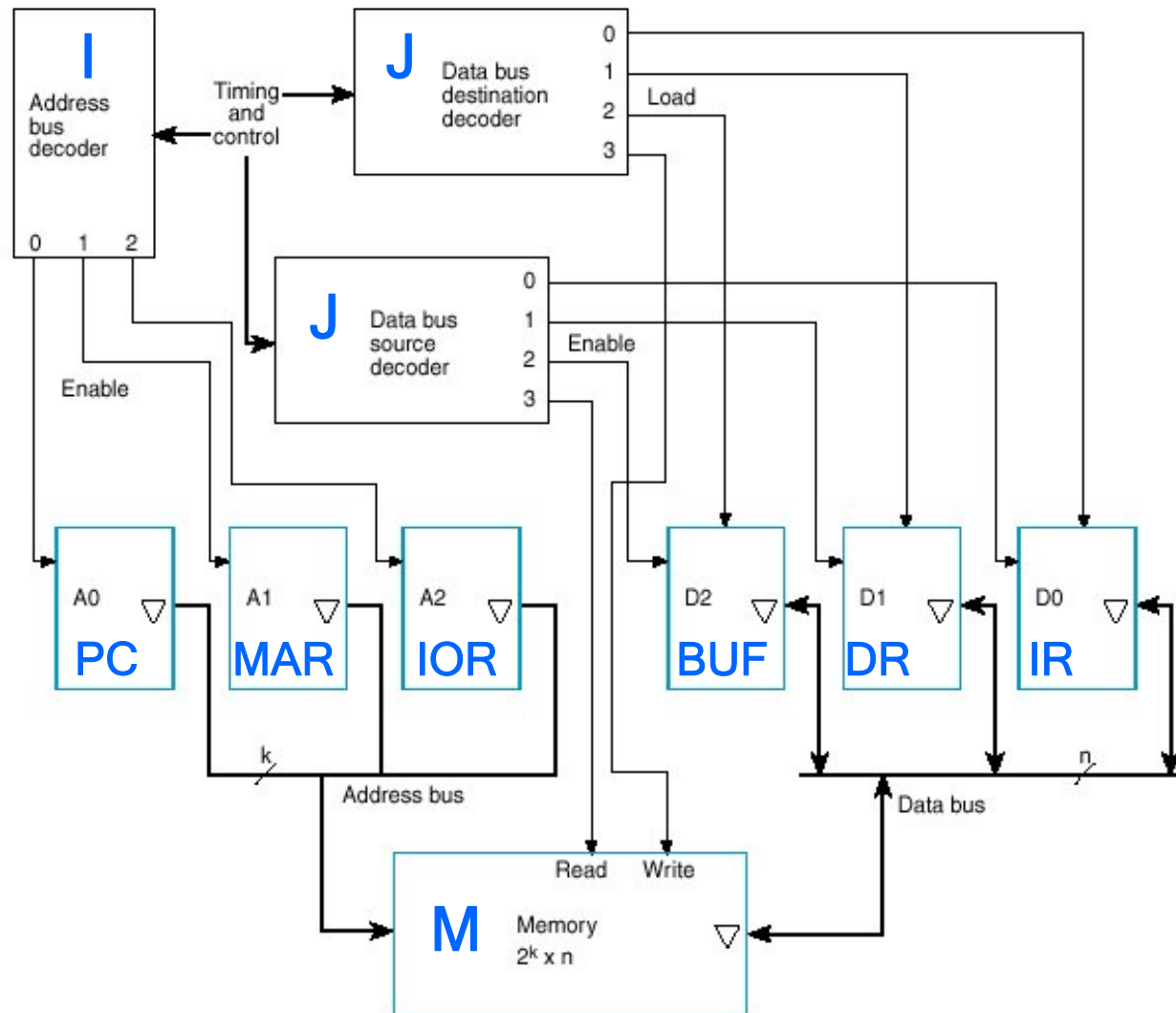$D[J] \leftarrow M[A[I]]$
 $M[A[I]] \leftarrow D[J]$



► In all digital systems we can partition the structure into two sections:

- The data path which performs data-processing operations on the data stream.
- The control unit which determines the schedule for these data processing operations.

Control Inputs

Control Unit

Control Outputs

Control Signals


Data Input

Datapath

Status Signals

Data Output

CS2022 Datapath Schematic

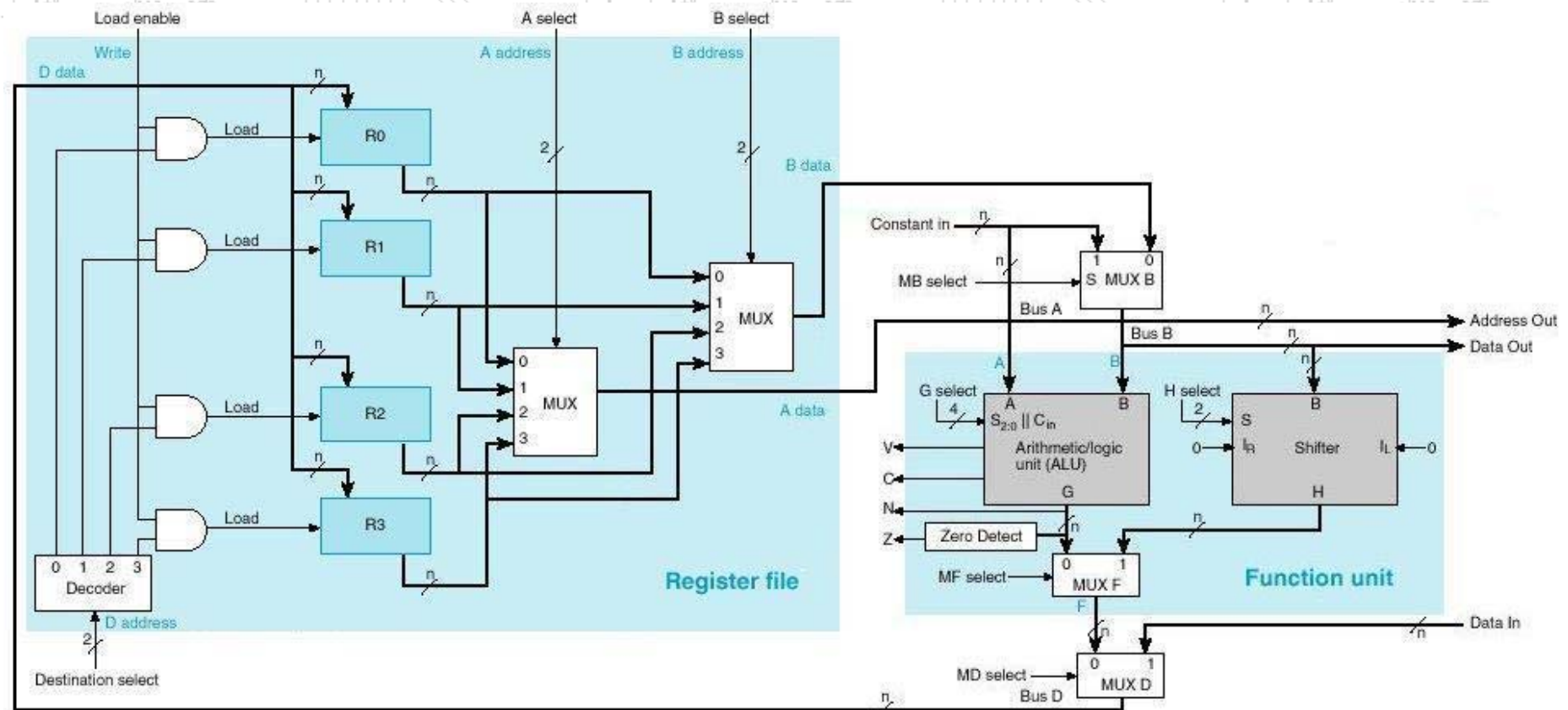

CS2022 Register File & Functional Unit

- ▶ In practice the three functional micro-ops are implemented in one compact circuit, the **Function Unit**, composed of the **ALU** and **Shifter**.
- ▶ Data for this **Function Unit** comes from a physical adjacent **Register file**, with dual MUX-busses able to supply two operands per clock cycle.
- ▶ Since the register file is itself modest in size typically 8-32 register, there must be provision to send and receive data to/from the main memory system via **DATA IN** and **DATA OUT**.