

- ▶ When we use fixed size Register for arithmetic operands there is the hazard at each micro-ops of overflow.
- ▶ If Register R stores an n-bit 2's complement number, then:

$$-2^{n-1} \leq R \leq 2^{n-1}-1$$


- ▶ Note the asymmetry, so even negation can cause overflow, e.g.

$$R \leftarrow -2^{n-1} \text{ then } R \leftarrow -R \Rightarrow \text{OVERFLOW}$$

CS2022 Carry and Overflow

- We can detect overflow for all the previous operations simply by recording the status bits C = Carry and V = Overflow (see section 3.10 I Mano and Kime).
 
$$K_1: C \leftarrow C_n, V \leftarrow C_n \oplus C_{n-1}$$



CS2022 Adder-Subtractor


- ▶ This then is the basis for the adder-subtractor on the next page which uses control input X to select addition and X for subtraction.

$$\bar{X}.K_1: R1 \leftarrow R1 + R2$$

$$X.K_1: R1 \leftarrow R1 + \overline{R2} + 1$$

$$K_1: C \leftarrow C_n, V \leftarrow C_n \oplus C_{n-1}$$

CS2022 Add & Subtract Micro operation

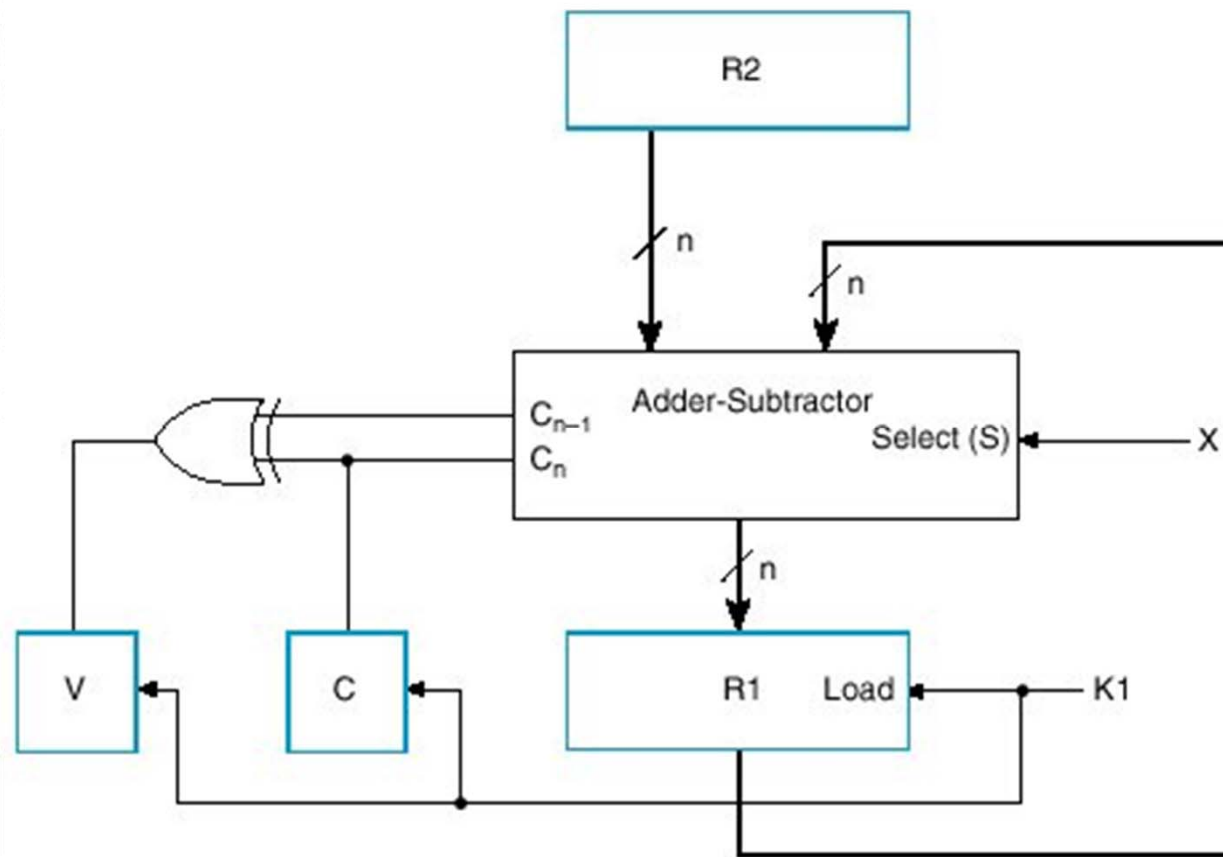

CS2022 Logic Micro-operations

▶ The aim here is to provide an effective set of bit-wise functions. A typical basic set follows:

**Symbolic
micro-op**

Description

$R0 \leftarrow \overline{R1}$

Logical bitwise NOT (1's compliment)

$R0 \leftarrow R1 \wedge R2$

Logical bitwise AND (clears bits)

$R0 \leftarrow R1 \vee R2$

Logical bitwise OR (sets bits)

$R0 \leftarrow R1 \oplus R2$

Logical bitwise XOR (complements bits)

CS2022

^ And v

- ▶ George Bode Prof. Of mathematics in UCC introduced the notation ' \wedge ' and ' \vee ' in 1854, and they are used in Register Transfer (RT) notation if it is necessary to distinguish addition from logical OR. For example:

$K_1 + K_2 : R1 \leftarrow R2 + R3, R4 \leftarrow R5 \vee R6$

Logical OR

Logical OR

addition

- ▶ The OR micro-ops will always use \vee .

CS2022 Shift Micro-operations

- ▶ These provide lateral bitwise shift which are essential for many basic arithmetic algorithms e.g. multiplication division, square root...
- ▶ The minimal set is:

$$\begin{aligned} R \leftarrow sr \ R &\equiv R_i \leftarrow R_{i+1} \ i=0, n-2, R_{n-1} \leftarrow 0 \\ R \leftarrow sl \ R &\equiv R_i \leftarrow R_{i-1} \ i=1, n-1, R_0 \leftarrow 0 \end{aligned}$$

CS2022 Logical Shifts

- ▶ These are logical shifts and from them you can develop variants which handle the end bits differently, e.g. arithmetic shift, rotates...
- ▶ Please see table 9-5 in Mano and Kime.

CS2022 Transfer Micro-operations

- ▶ Providing choice of path
- ▶ Two approaches are used:
 - ▶ Multiplexer-based transfer for speed
 - ▶ Bus-based transfers for flexibility and economy

CS2022 Transfer with Multiplexer

- ▶ The if-then else control structure, when applied to identity micro-ops, results in the destination register requiring selective access to two different source registers.

If ($K_1=1$) then $R0 \leftarrow R1$
else if ($K_2=1$) then $R0 \leftarrow R2$

$K_1: R0 \leftarrow R1, \bar{K}_1 K_2: R0 \leftarrow R2$

CS2022 Two Sources - One Destination


- ▶ To route two sources to one destination we can use a **2:1 MUX** with control input **S**, data input **$D0 \wedge D1$** , and R0 must have a load control **$LOAD_{R0}$** .
- ▶ From the RT description we deduce the following functions for these control inputs.

$$LOAD_{R0} = K_1 + \bar{K}_1 K_2 = K_1 + K_2$$
$$S = K_1 \Rightarrow D1 = R1 \wedge D0 = R2$$

CS2022

Multiplexer

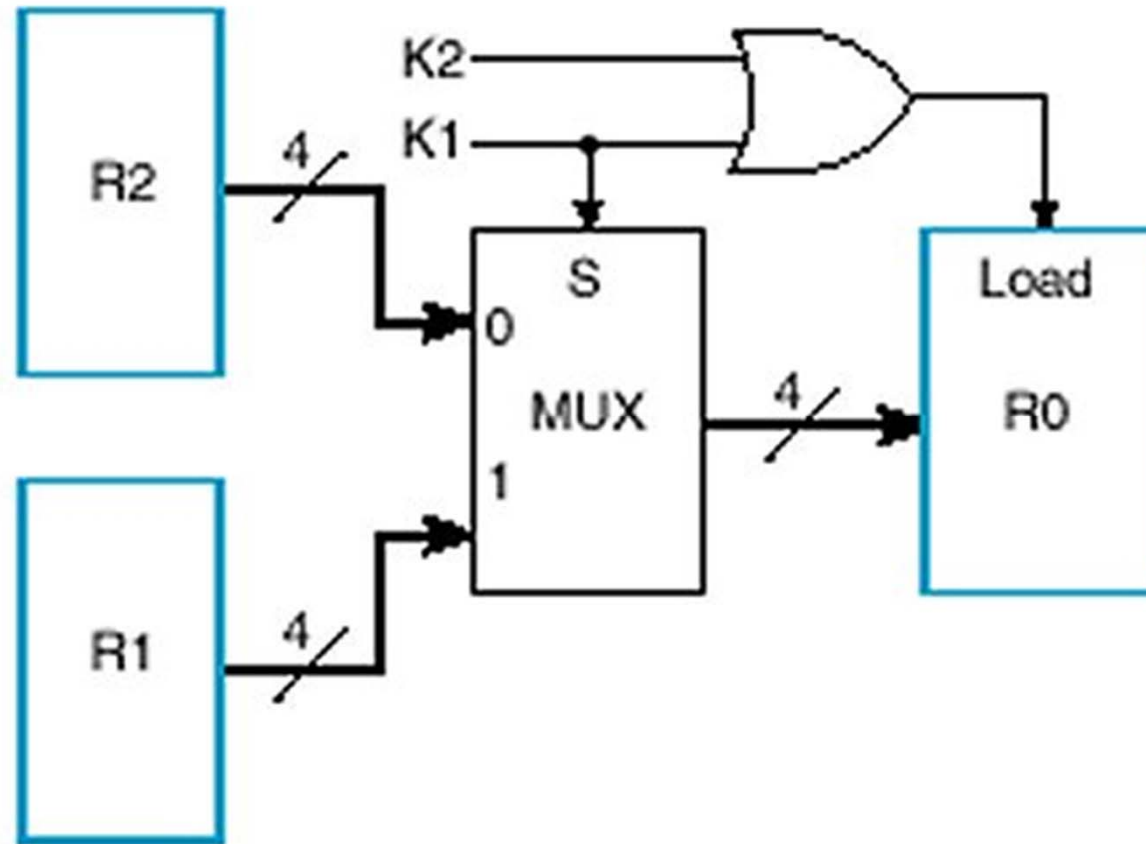- ▶ From this we derive the circuit schematic, assuming 4-bit Registers.



CS2022 Multiplexer Detail

► Note changes in K1 only affect the MUX – R0 path, so transients are short, allowing fast operation.

